



CENG 3420

Computer Organization & Design

Lecture 08: Datapath

Textbook: Chapter 4.1-4.4

Zhengrong Wang

CSE Department, CUHK

zhengrongwang@cuhk.edu.hk




Overview



Processor Overview

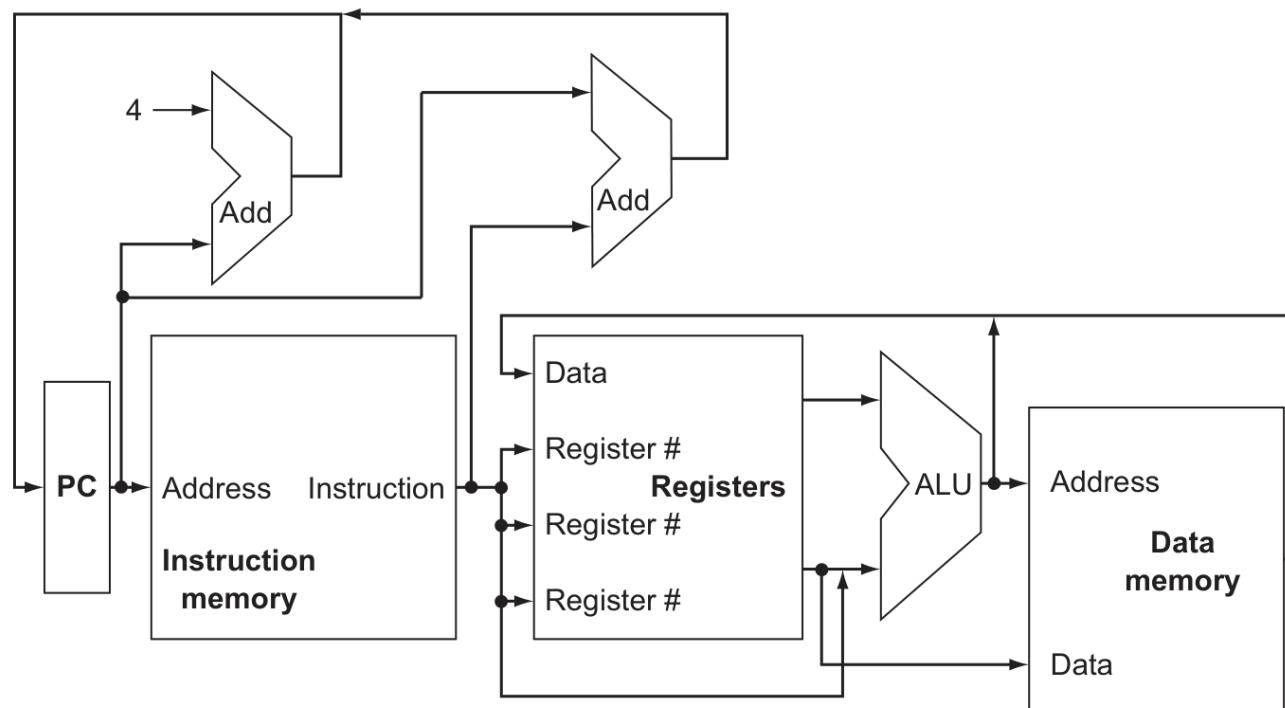
- Get instruction from instruction memory at PC (program counter).
- Get source operands from register or immediate number in the instruction.
- Perform the operation, e.g. add, load from memory, store to memory, take a branch.
- Update PC to next instruction (+4 if no branch), and repeat from Step 1.





Implement Minimal RISC-V

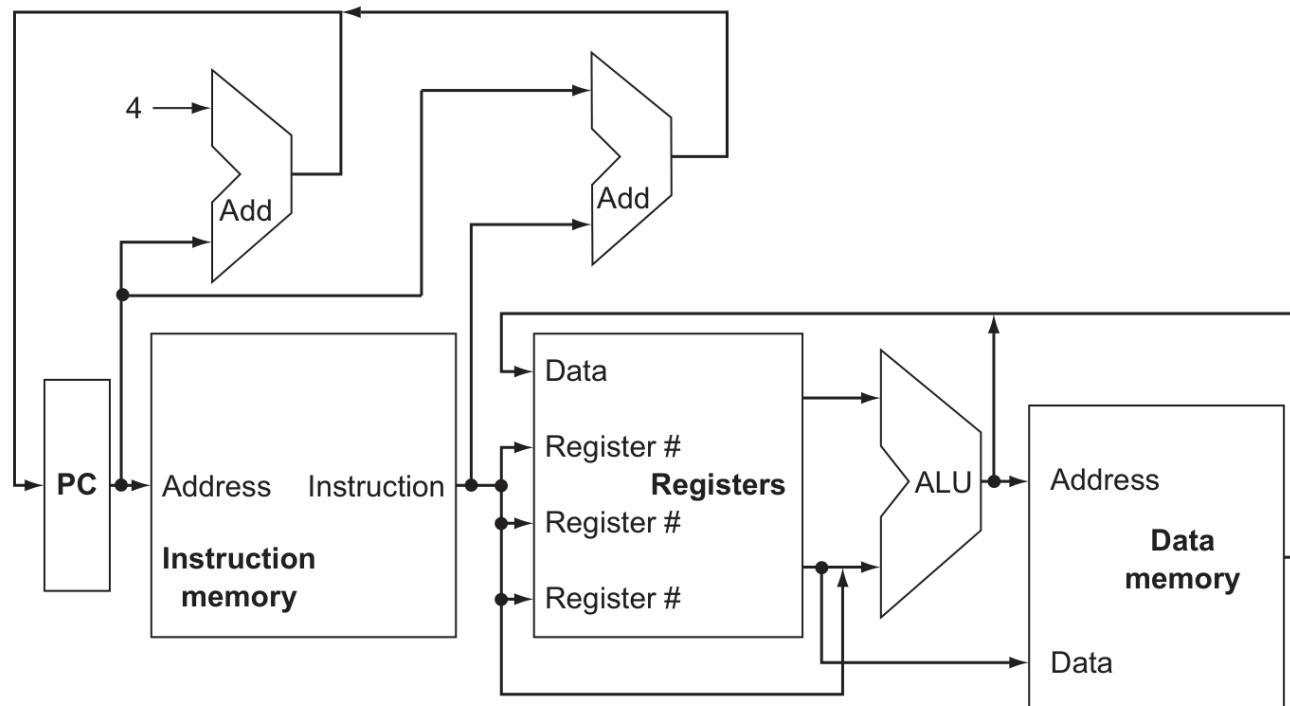
- Arithmetic-logic instructions: add, sub, and, or.
- Memory reference instructions: lw (load word), sw (store word).
- Conditional branch instruction: beq (branch if equal).
- We will see how to add control signals to build datapath for these instructions!





Logic Design Conventions

- **Combinational** elements operates on data value:
 - Outputs only depends on the current inputs.
 - E.g., AND gate.
- **State** elements contains the state:
 - At least two inputs (new state and clock) and one output (old state).
 - At each clock edge (posedge or negedge), the state is updated.
- All elements have some latency – limits the frequency of the processor.
 - Otherwise, state element 2 may not yet get the correct value.

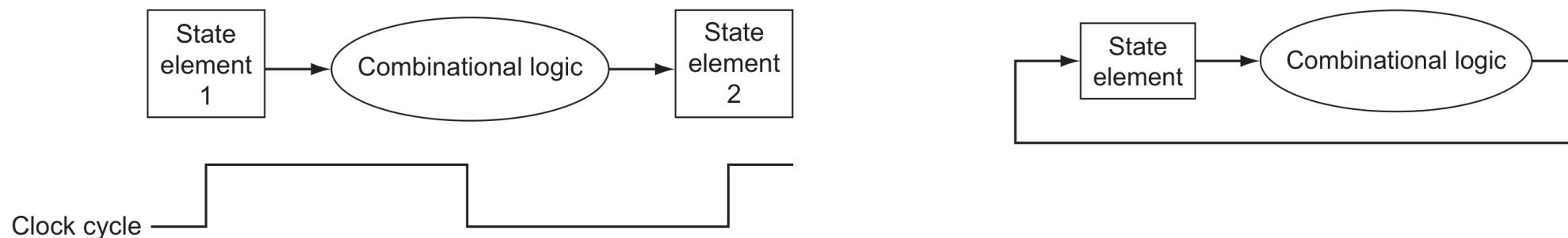




Simple Datapath




Instruction Fetch

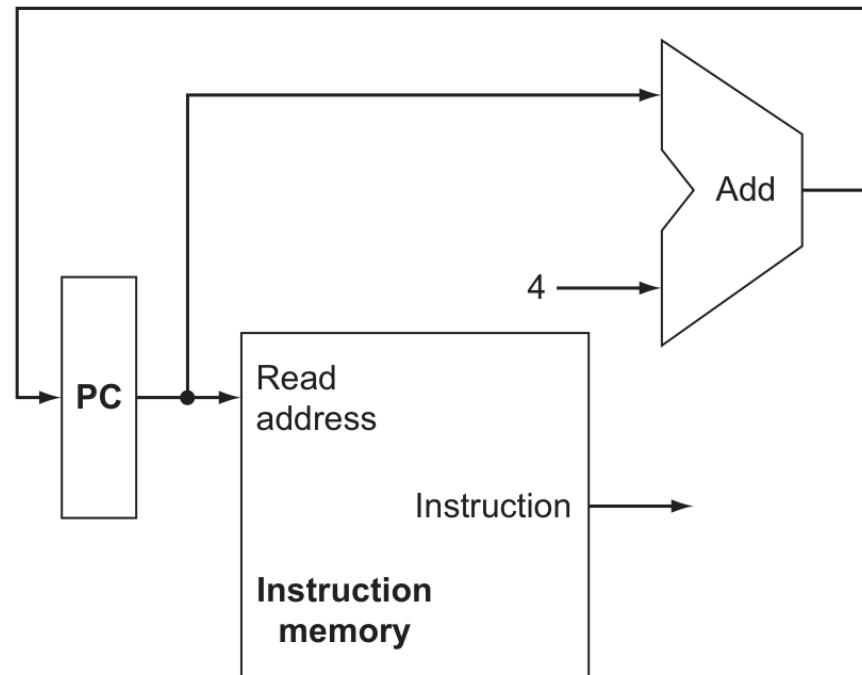- Three components: PC (state), instruction memory (state), adder.
 - Read one instruction at PC from the instruction memory.
 - Increment PC by 4 bytes (32-bit) for next instruction.
- Shared among all instructions.






R-Type Instructions

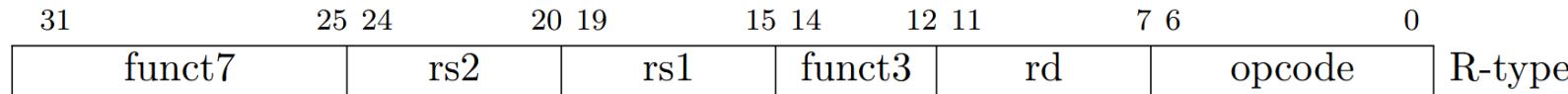

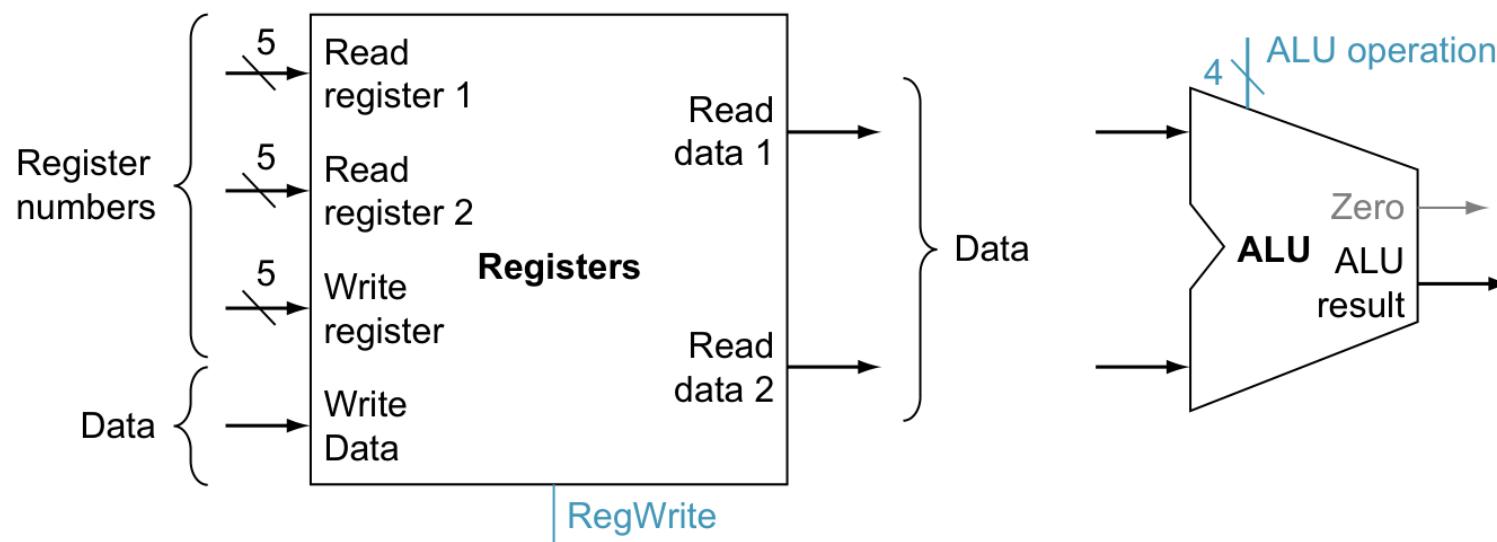- Always read two registers (rs1 and rs2) and write one register (rd).
- Besides fetching instructions, we need two more components.
 - **Register file**: Holds 32 32-bit value, with **RegWrite** controlling whether to write.
 - **ALU**: 4-bit ALU operation to control the behavior (add, sub, etc., see Lecture 06).






Memory Load and Store Instructions

imm[11:0]	rs1	funct3	rd	opcode	I-type	
imm[11:5]	rs2	rs1	funct3	imm[4:0]	opcode	S-type

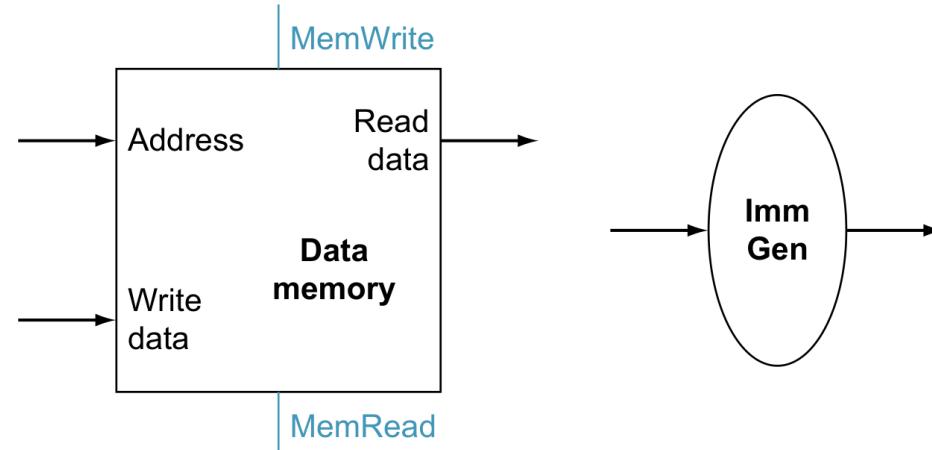- Load and store operations
 - **Sign-extend** 12-bit imm to 32-bit offset, **compute** address = base (in rs1) + offset.
 - For load, rd = memory[address]; For store, memory[address] = rs2.
- Besides ALU for address generation, we need two more components:
 - **Immediate generation unit** (Imm Gen) for sign-extension.
 - **Data memory unit** with read and write support.






Branch Instruction

imm[12]	imm[10:5]	rs2	rs1	funct3	imm[4:1]	imm[11]	opcode	B-type
---------	-----------	-----	-----	--------	----------	---------	--------	--------


- Branch if equal (beq) :
 - Jump if rs1 equals rs2.
 - Target address = PC + offset.
 - Offset from sign-extension of imm to 32-bit.
 - Note: offset is encoded in **factor of 2**, i.e., **imm[0] = 0** \rightarrow PC always aligns to 2-byte.
- Portion of the datapath for beq instruction
 - Imm Gen for sign-extension.
 - Register file for two compared operands.
 - ALU to test equality.
 - **Separate adder** to compute target address.

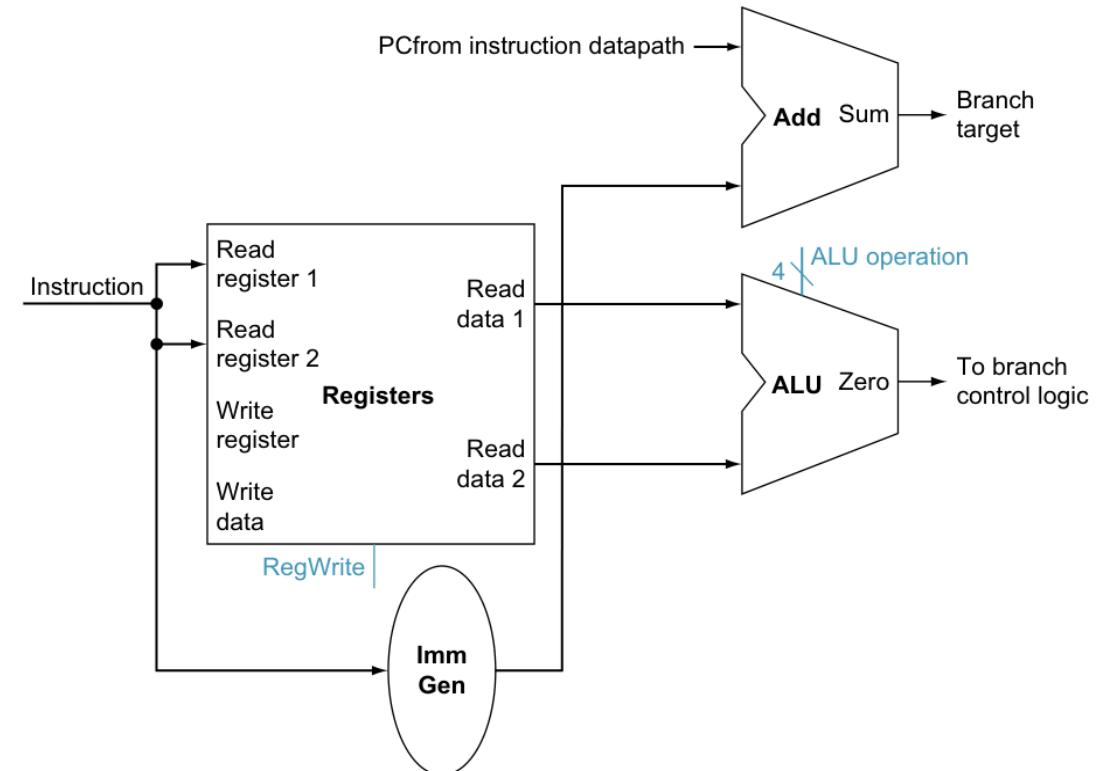




Shared Datapath

- Instructions **share** many components in their datapath.
 - They all use the ALU for some operation.
 - They all need PC and instruction memory.
 - They perform sign-extension on the immediate (except R-type instructions).
- We want to **reuse** components in their datapath.
 - Save hardware resources on area and power.
 - Increase hardware utilization.
- But we need to coordinate shared components.
 - E.g., 4-bit ALU op to dictate what operation the ALU to perform.
 - Essentially **multiplexors** to select value based on the control signal.

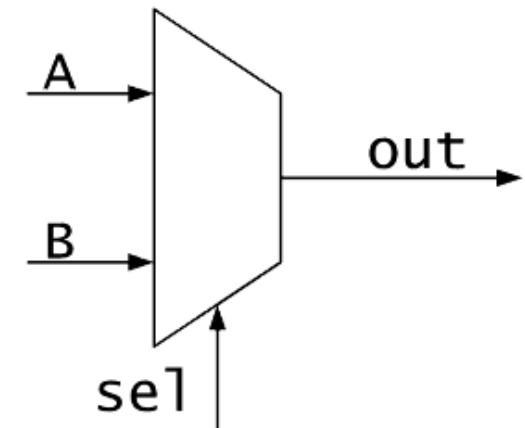




Combine R-Type and Memory Instructions

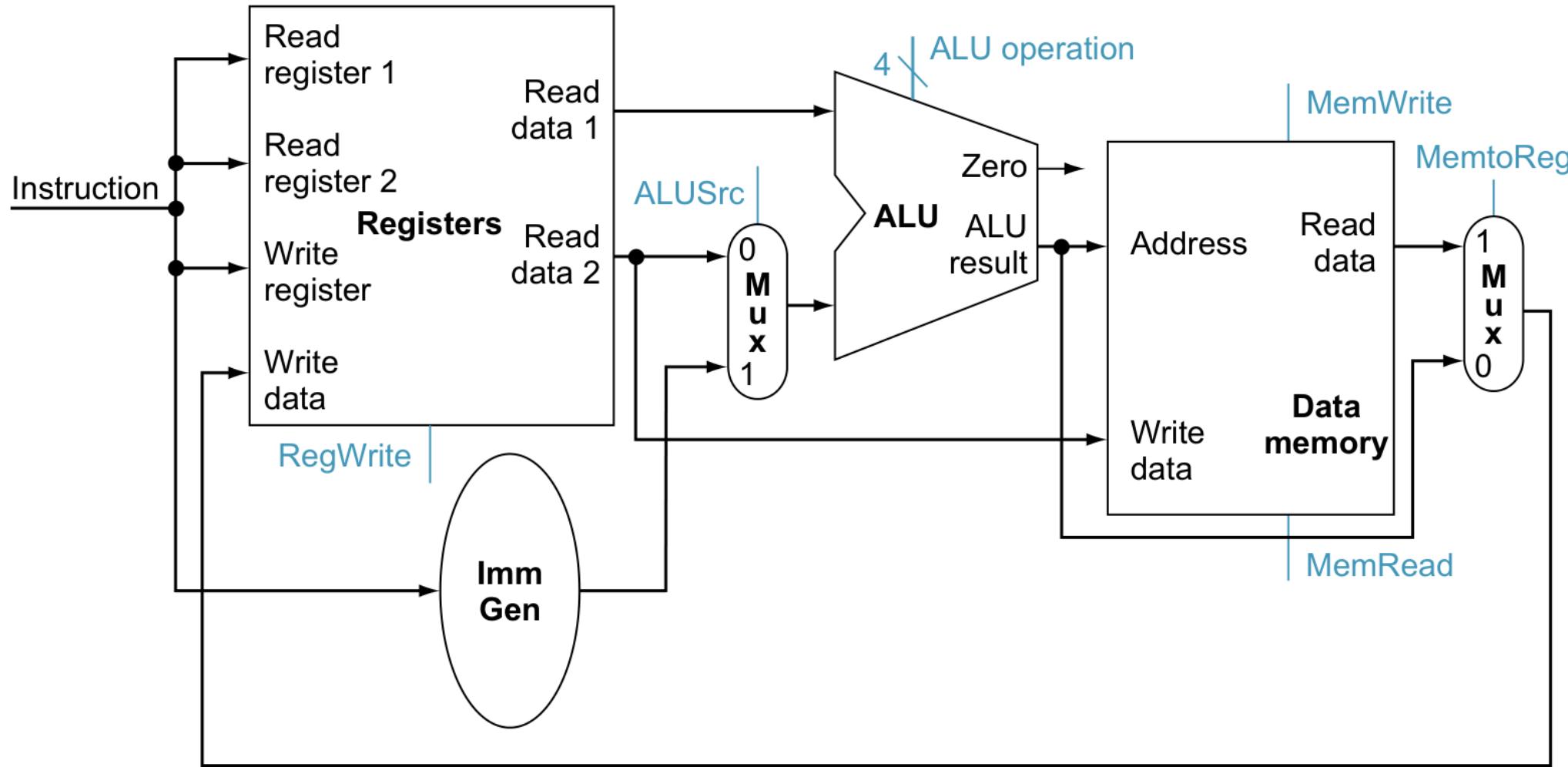




Combine R-Type and Memory Instructions

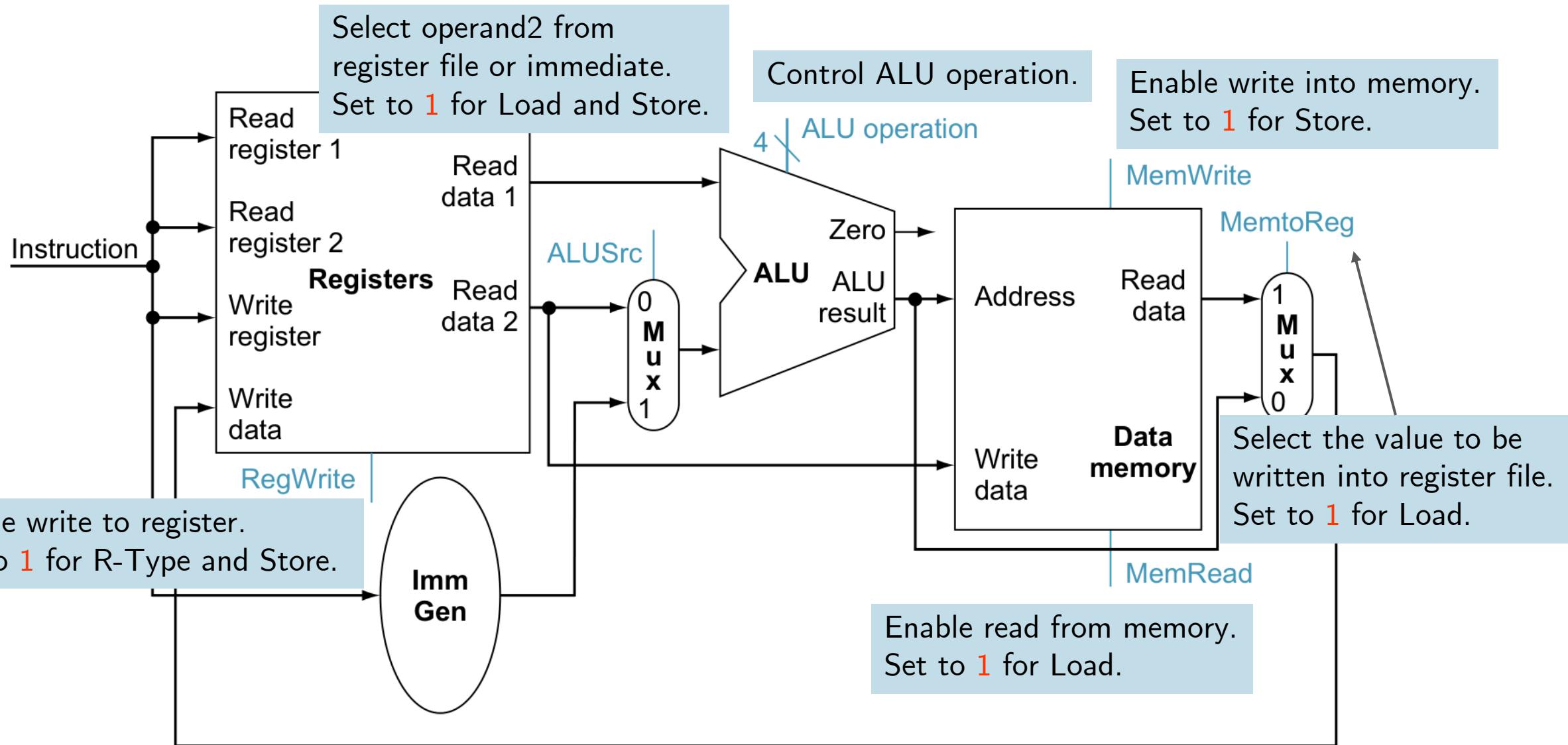



Add Branch Datapath

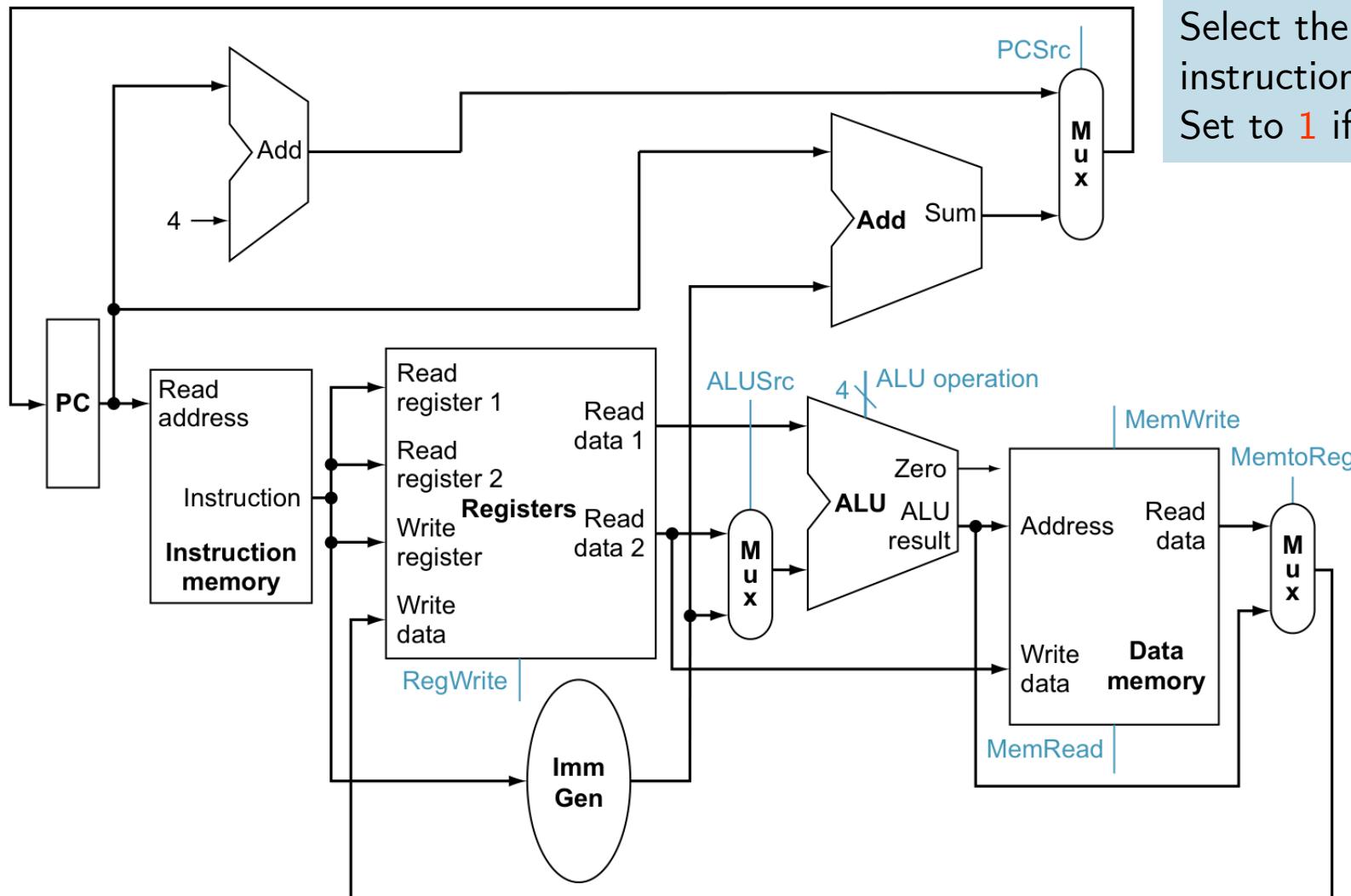




Control Unit



How to Generate Control Signals?

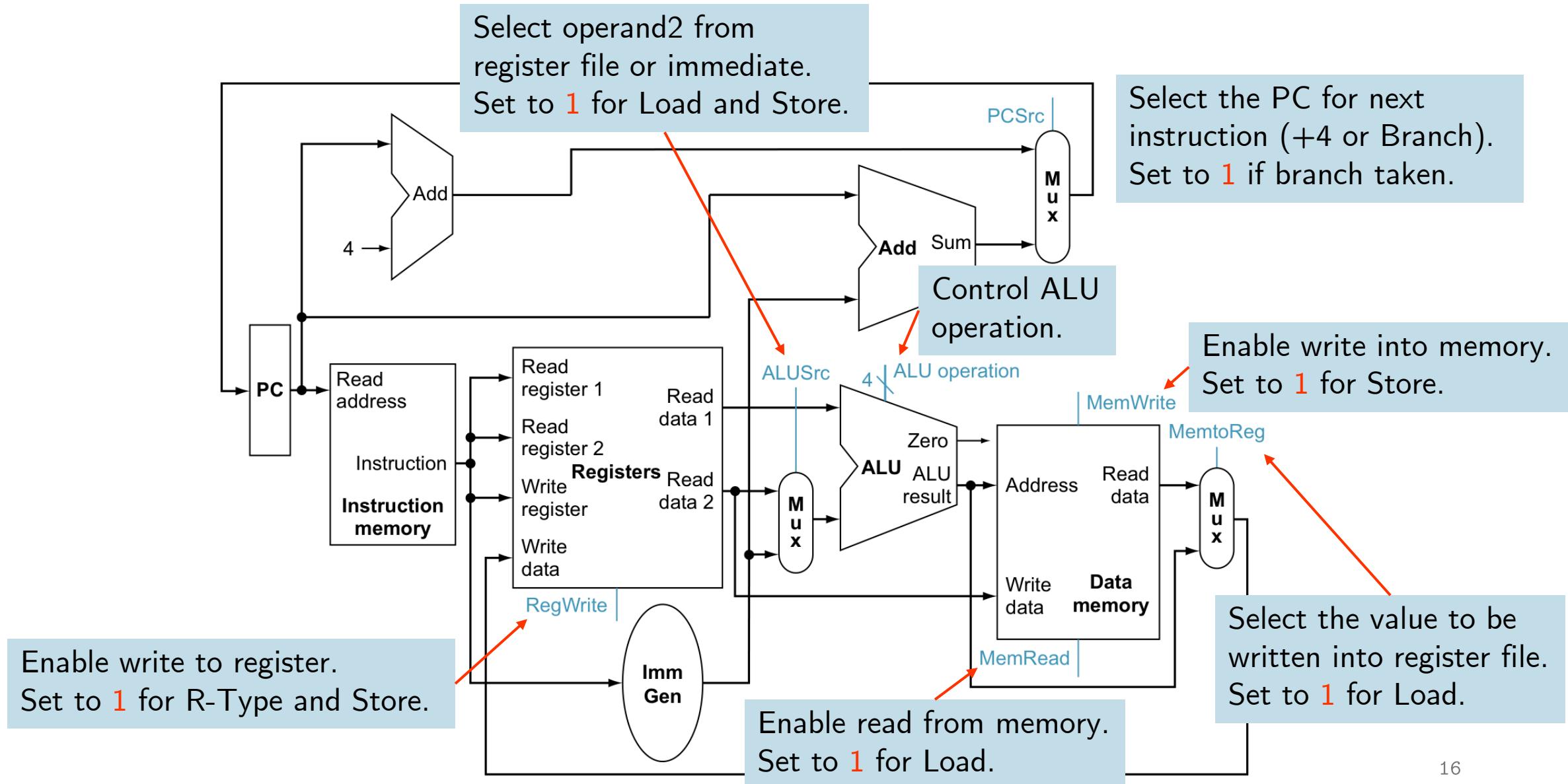



Detailed Meaning of Control Signals

- The main control unit need to set these based on instruction opcode/funct.

Signal name	Effect when deasserted	Effect when asserted
RegWrite	None.	The register on the Write register input is written with the value on the Write data input.
ALUSrc	The second ALU operand comes from the second register file output (Read data 2).	The second ALU operand is the sign-extended, 12 bits of the instruction.
PCSrc	The PC is replaced by the output of the adder that computes the value of $PC + 4$.	The PC is replaced by the output of the adder that computes the branch target.
MemRead	None.	Data memory contents designated by the address input are put on the Read data output.
MemWrite	None.	Data memory contents designated by the address input are replaced by the value on the Write data input.
MemtoReg	The value fed to the register Write data input comes from the ALU.	The value fed to the register Write data input comes from the data memory.



Two-Level Control Logic for ALU

- Two-level control logic: main control unit → ALU control unit → ALU.
 - Main control unit generates 2-bit ALUOp based on instruction type.
 - ALU control unit generates 4-bit ALU control based on ALUOp and funct.
- Simplifies hardware complexity → less latency → higher frequency.
 - Main control unit only checks opcode field.
 - ALU control unit only checks funct7 and func3 for R-type.

Instruction opcode	ALUOp	Operation	Funct7 field	Funct3 field	Desired ALU action	ALU control input
lw	00	load word	XXXXXXX	XXX	add	0010
sw	00	store word	XXXXXXX	XXX	add	0010
beq	01	branch if equal	XXXXXXX	XXX	subtract	0110
R-type	10	add	0000000	000	add	0010
R-type	10	sub	0100000	000	subtract	0110
R-type	10	and	0000000	111	AND	0000
R-type	10	or	0000000	110	OR	0001



Observation on Instruction Format


31	30	25 24	21 20	19	15 14	12 11	8	7	6	0
funct7		rs2		rs1	funct3		rd		opcode	R-type
	imm[11:0]			rs1	funct3		rd		opcode	I-type
imm[11:5]		rs2		rs1	funct3	imm[4:0]		opcode		S-type
imm[12]	imm[10:5]		rs2	rs1	funct3	imm[4:1]	imm[11]	opcode		B-type

- The **opcode** field is always in bits 6:0. Depending on the opcode, the **funct3** field (bits 14:12) and **funct7** field (bits 31:25) serve as an extended opcode field.
- The first register operand is always in bit positions 19:15 (**rs1**) for R-type and branch instructions. This field also specifies the base register for load and store instructions.
- The second register operand is always in bit positions 24:20 (**rs2**) for R-type and branch instructions. This field also specifies the register operand that gets copied to memory for store.
- Another operand can also be a 12-bit **offset** for branch or load-store instructions.
- The destination register is always in bit positions 11:7 (**rd**) for R-type and load instructions.



Simple Datapath with Control Unit

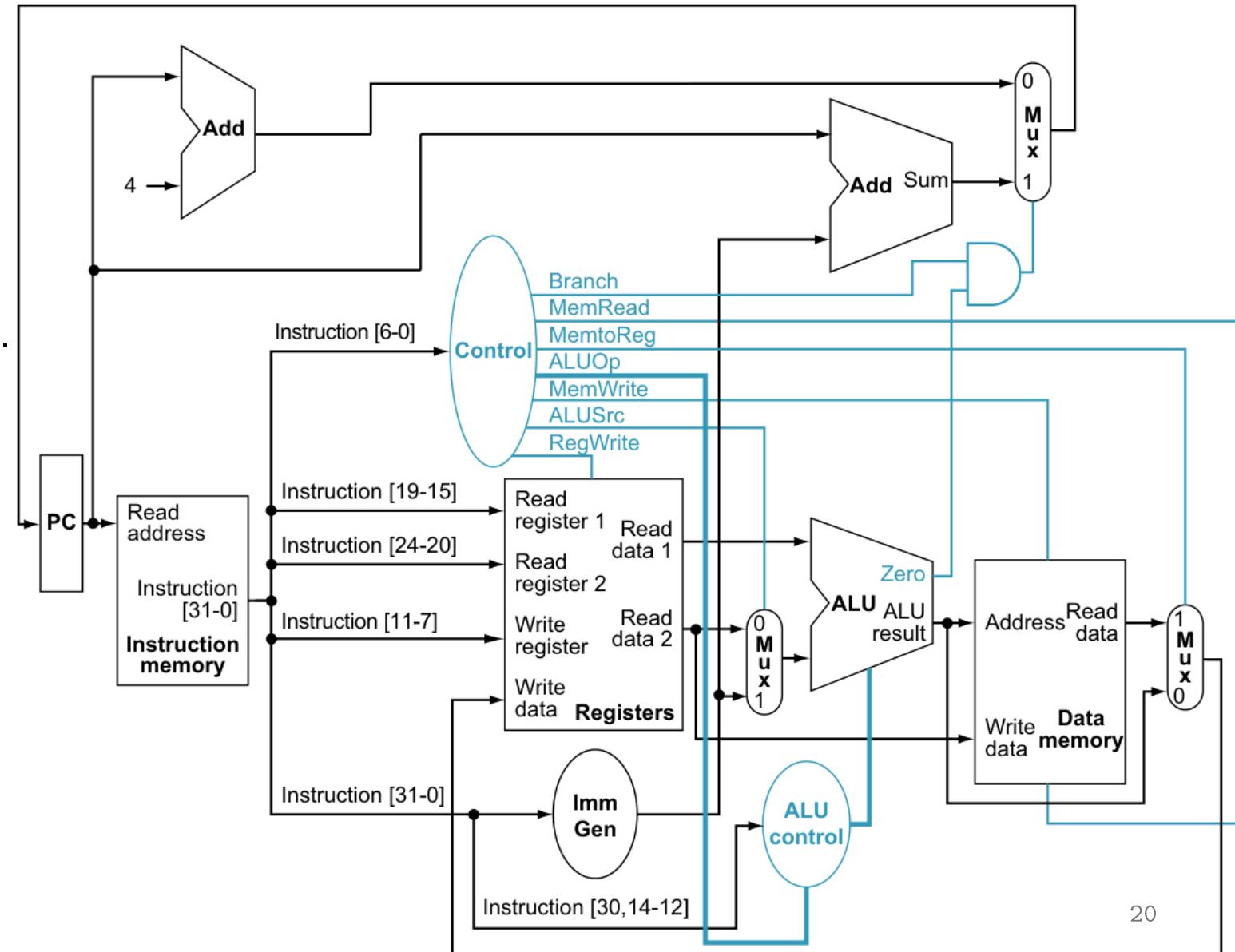
- Main control unit.
- ALU control.
- 2-bit ALUOp.
- 4-bit ALU control.
- Other control signals are 1-bit.
- Let's see some examples.





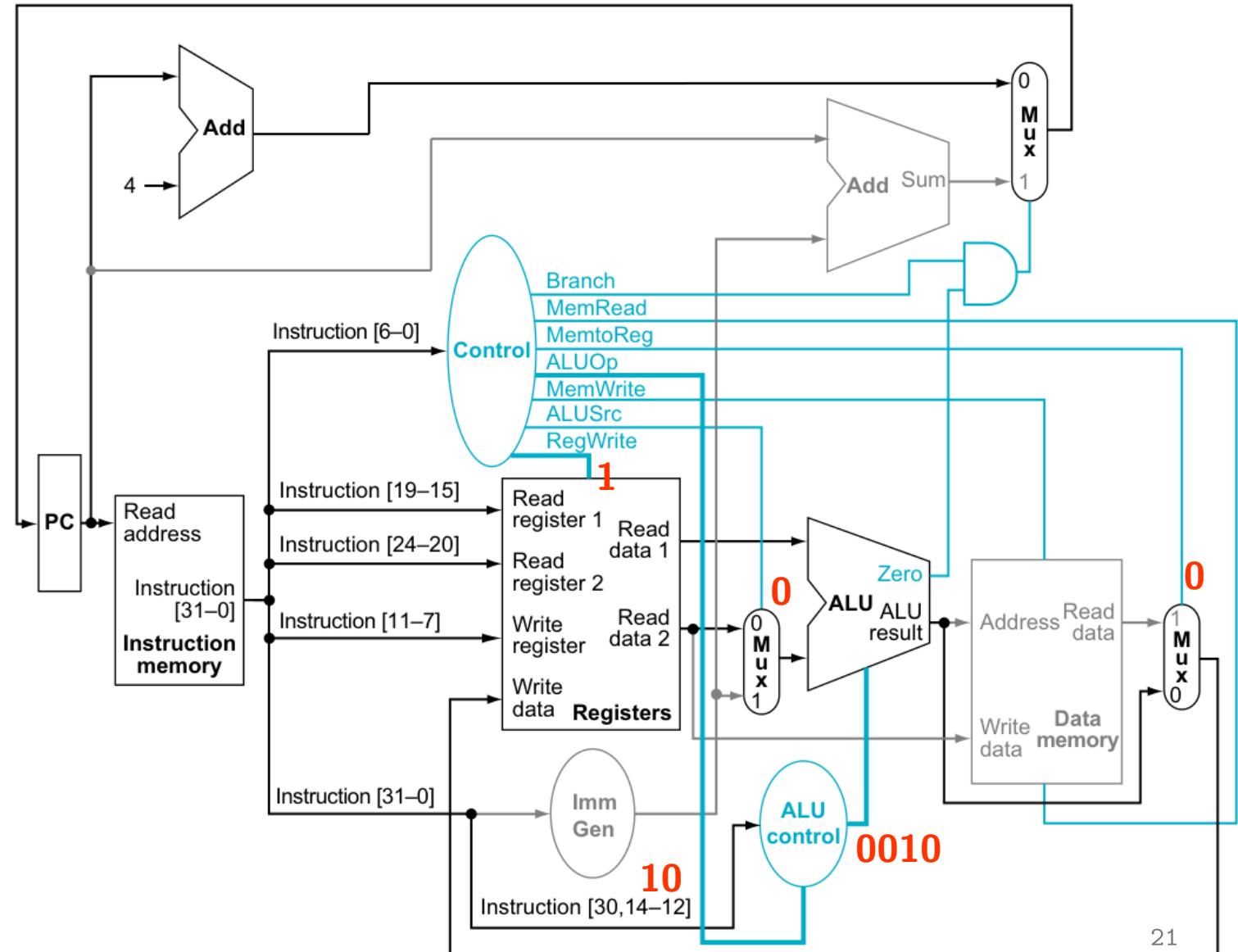Example: R-Type of add x1, x2, x3


- Black line – selected data.
- Gray line – unselected data
- $ALUOp = 10$ (R-type)
- $ALUControl = 0010$ (add)
- $ALUSrc = 0$
 - 2nd operand from rs2.
- $MemtoReg = 0$
 - Result from ALU
- $RegWrite = 1$
 - Write to rd.
- $Others = 0$
 - Not load/store/branch.





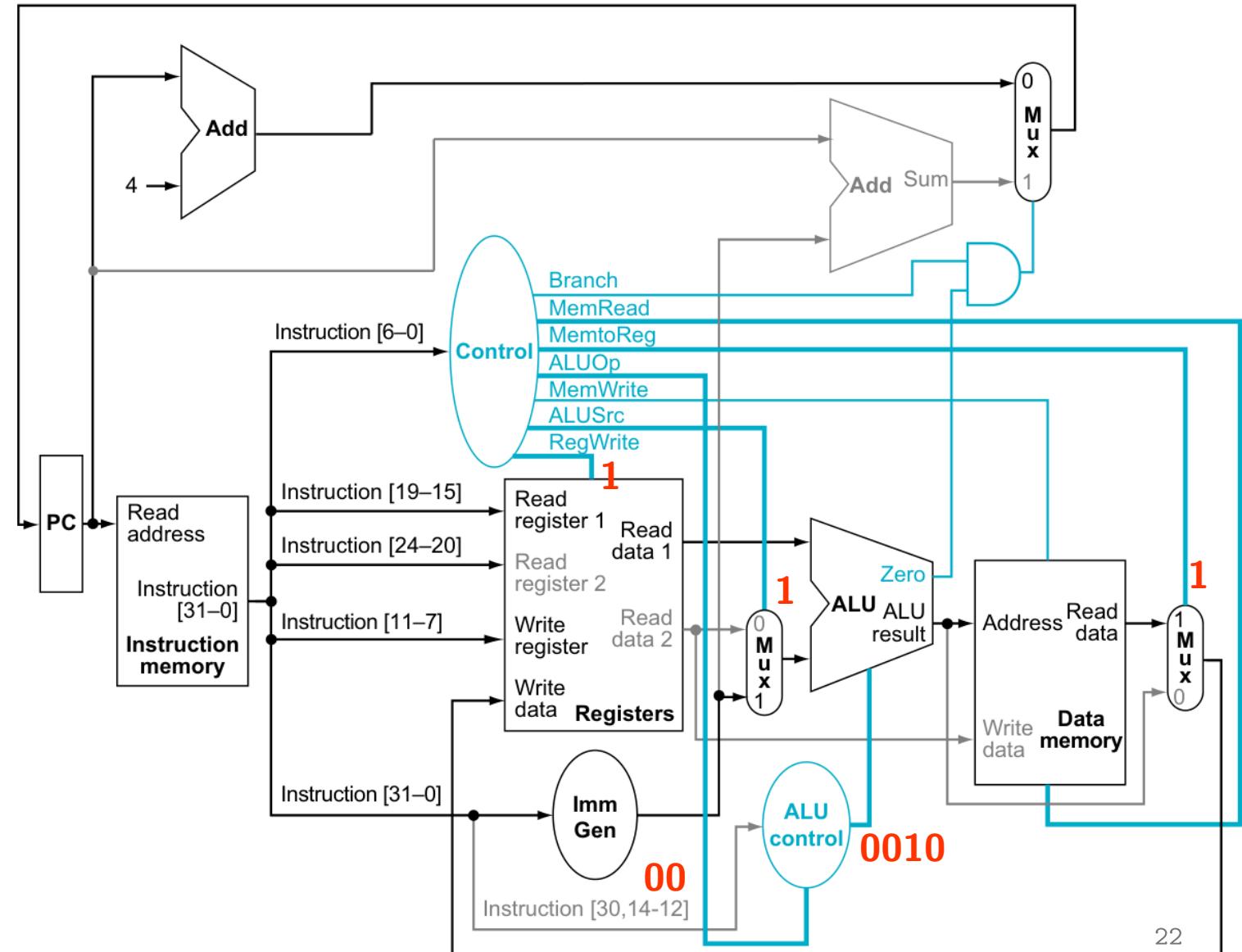Example: Load Instruction


- Black line – selected data.
- Gray line – unselected data.
- $ALUOp = 00$ (lw/sw)
- $ALUControl = 0010$ (add)
- $ALUSrc = 1$
 - 2nd operand from imm.
- $MemRead = 1$
 - To read from memory
- $MemtoReg = 1$
 - Result from memory
- $RegWrite = 1$
 - Write to rd.





 Example: Branch Instruction


- Black line – selected data.
- Gray line – unselected data.
- $ALUOp = 01$ (beq)
- $ALUControl = 0110$ (sub)
- Branch = 1
 - And with zero.
 - Pick update PC.





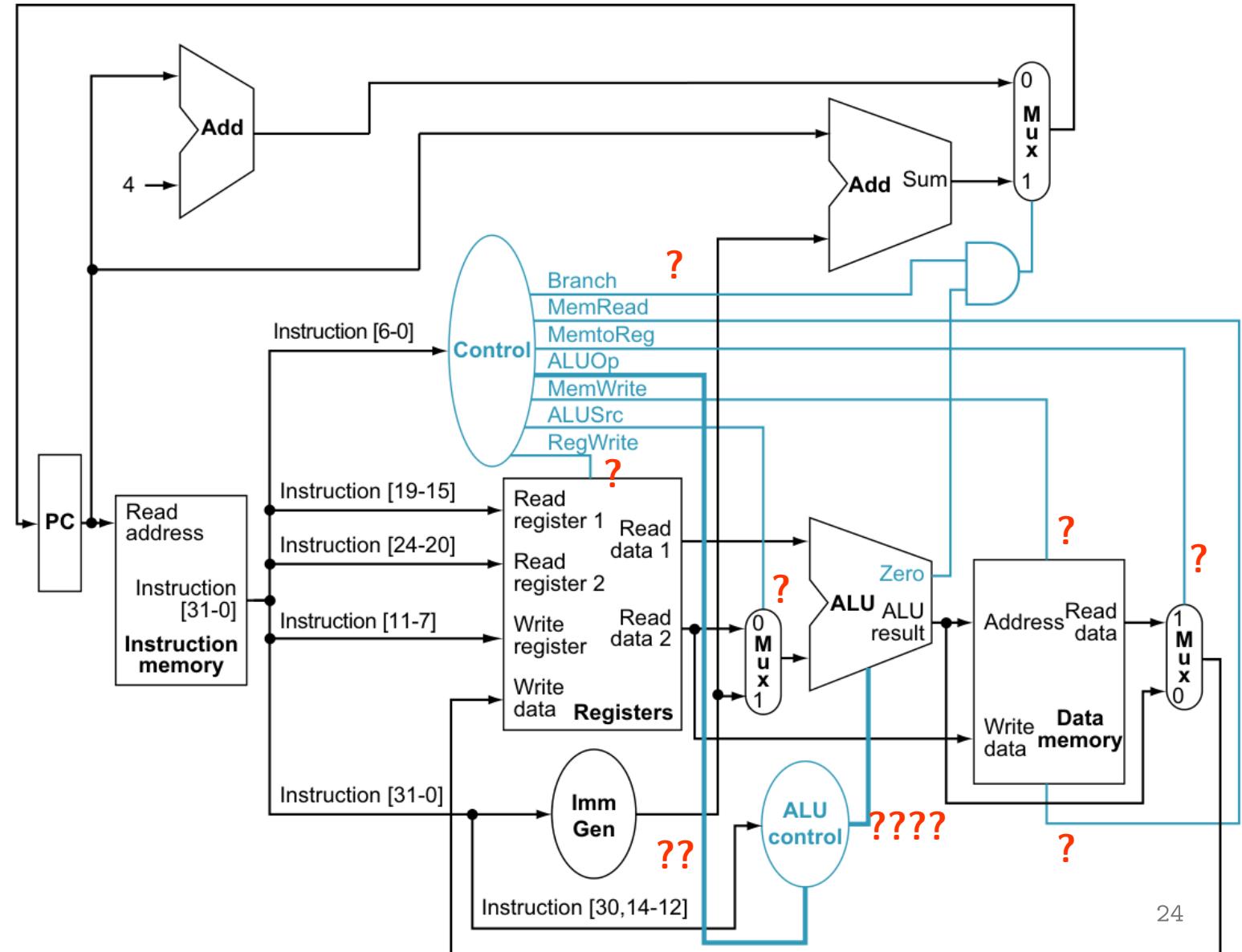Exercise: Show Control Signals of Store


- What sw does
 - Extend imm to offset.
 - Add offset with rs1.
 - Write rs2 to memory.
- What are the signals?





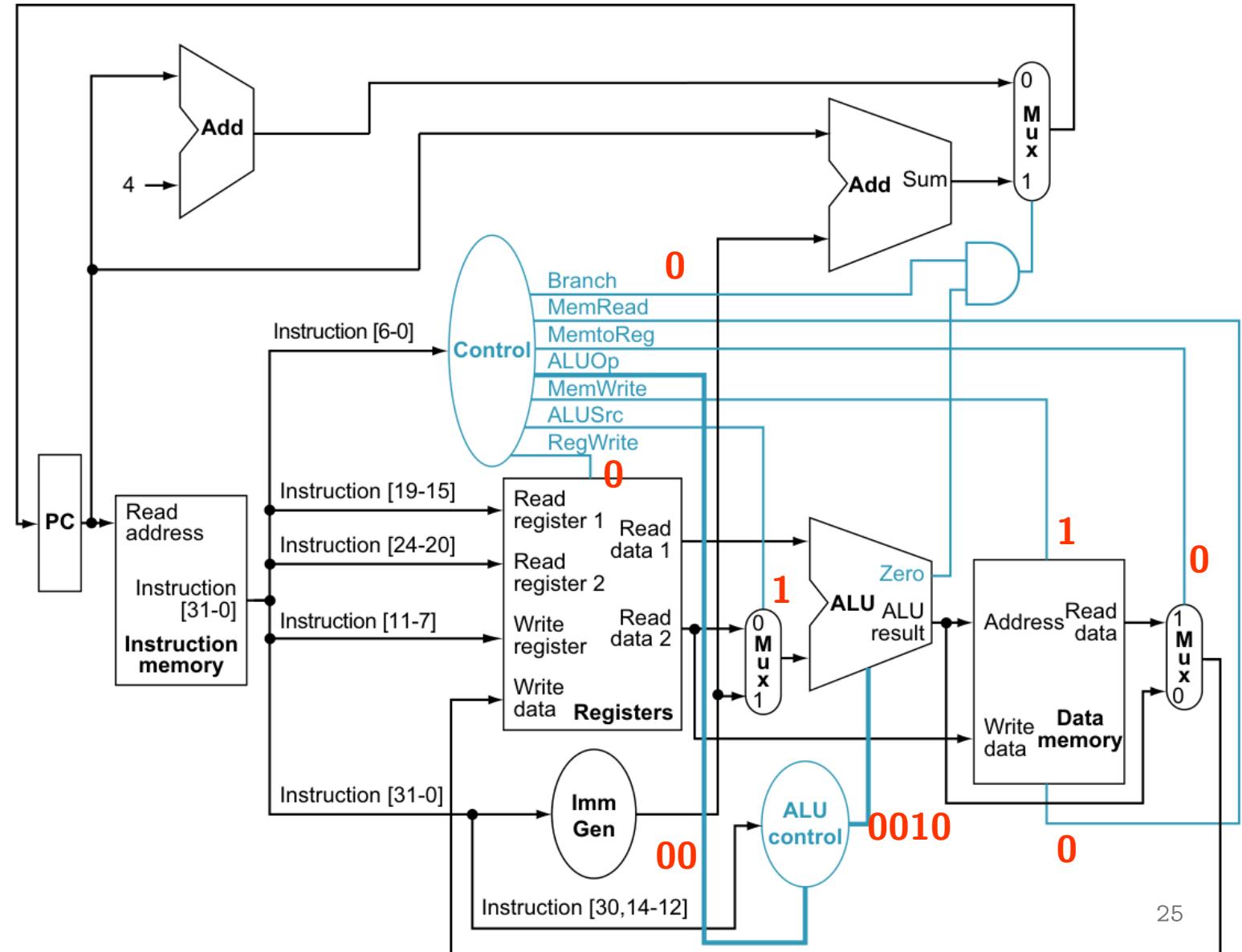Exercise: Show Control Signals of Store

- ALUOp = 00 (lw/sw)
- ALUControl = 0010 (add)
- ALUSrc = 1
 - 2nd operand from imm.
- MemWrite = 1
 - Write to memory





Summarize Main Control Unit

- Generate control signals based on instruction opcode (bit 0-6).
- Final truth table of main control unit:

Input or output	Signal name	R-format	lw	sw	beq
Inputs	I[6]	0	0	0	1
	I[5]	1	0	1	1
	I[4]	1	0	0	0
	I[3]	0	0	0	0
	I[2]	0	0	0	0
	I[1]	1	1	1	1
	I[0]	1	1	1	1
Outputs	ALUSrc	0	1	1	0
	MemtoReg	0	1	X	X
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1